

Assignment 2

DIGITAL IC DESIGN I

EE4610

Authors:

Senquan Zhang (6338216)

Yaonan Hu (6573657)

Daniel Tyukov (5714699)

January 12, 2026

Contents

1 Schematic 2

2 Results 4

2.1 Propagation delay 4

2.1.1 A-S route 5

2.1.2 B-S route 6

2.1.3 C-S route 7

2.1.4 A-Cout short route 8

2.1.5 A-Cout long route 9

2.1.6 C-Cout route 10

2.1.7 Data analysis 11

2.2 Quiescent power 12

2.3 Dynamic power 12

1 Schematic

This chapter will show the schematics of the full adder we designed. For the simulation we use default processing speed.

Design details:

PMOS: width=2 μm ; length=180 nm ; NMOS: width=1 μm ; length=180 nm

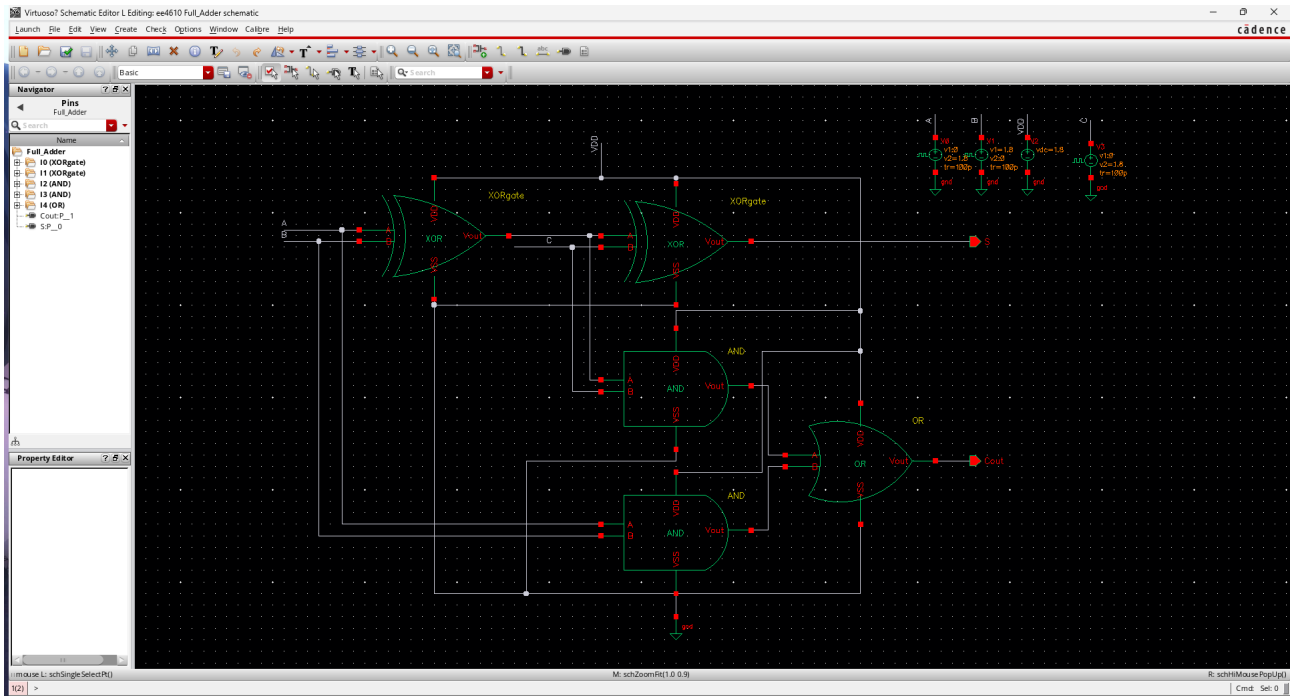


Figure 1: Full adder schematic.

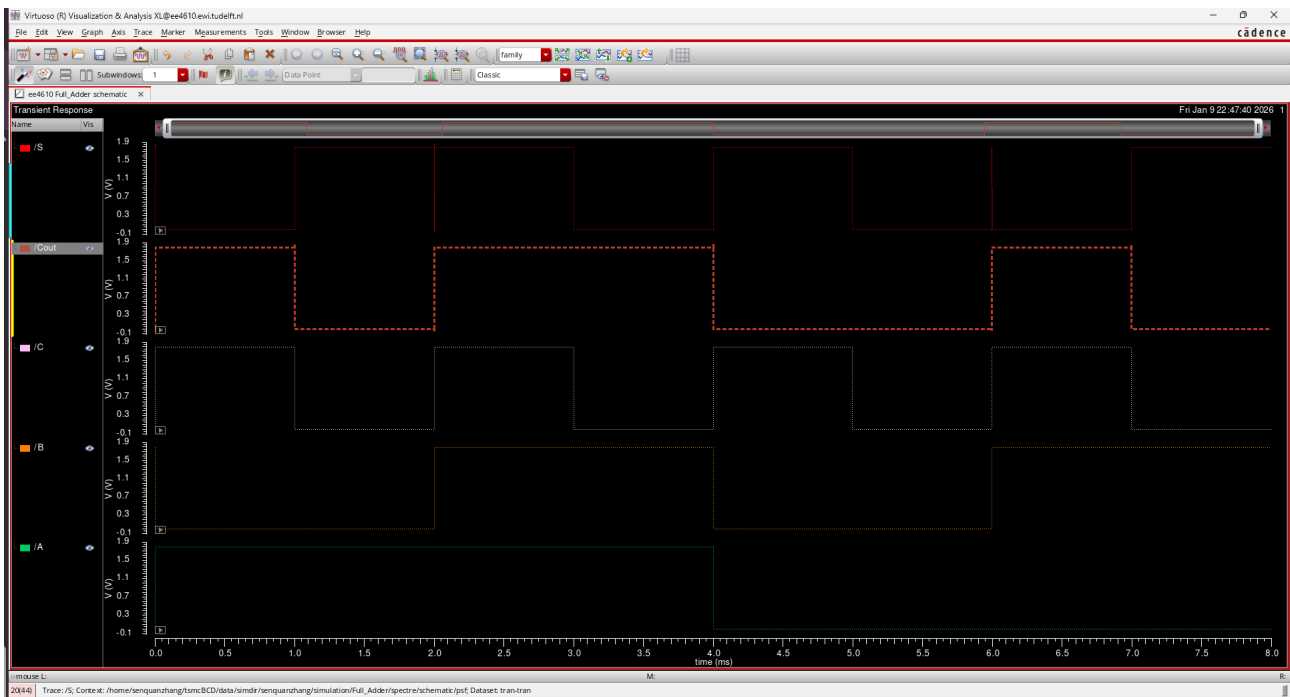


Figure 2: Full adder functional verification (inputs: A, B, C; outputs: S, Cout).

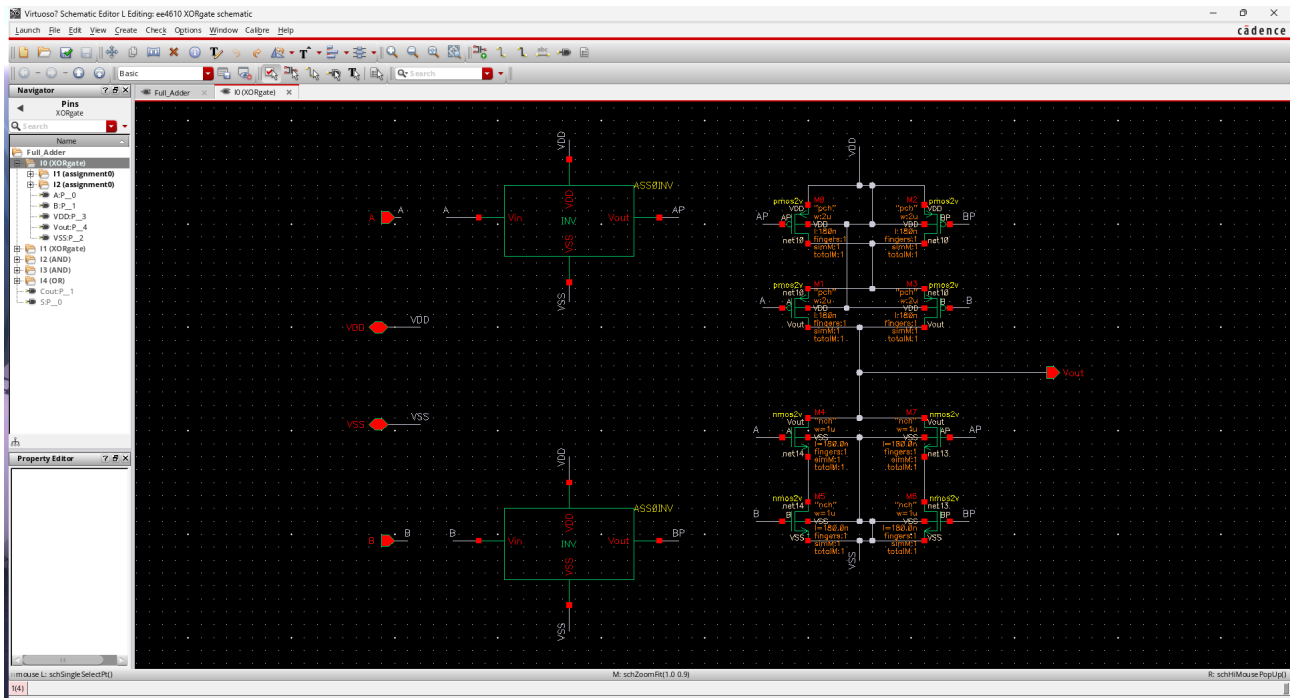


Figure 3: XOR gate schematic.

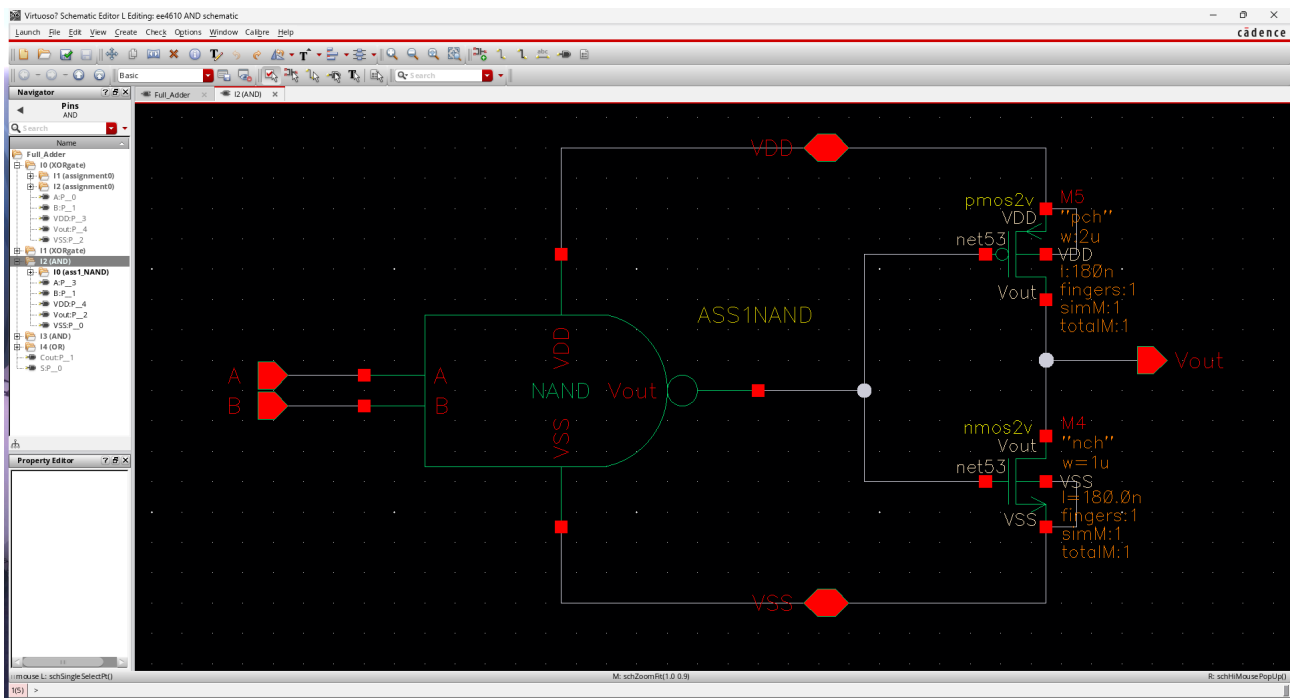


Figure 4: AND gate schematic.

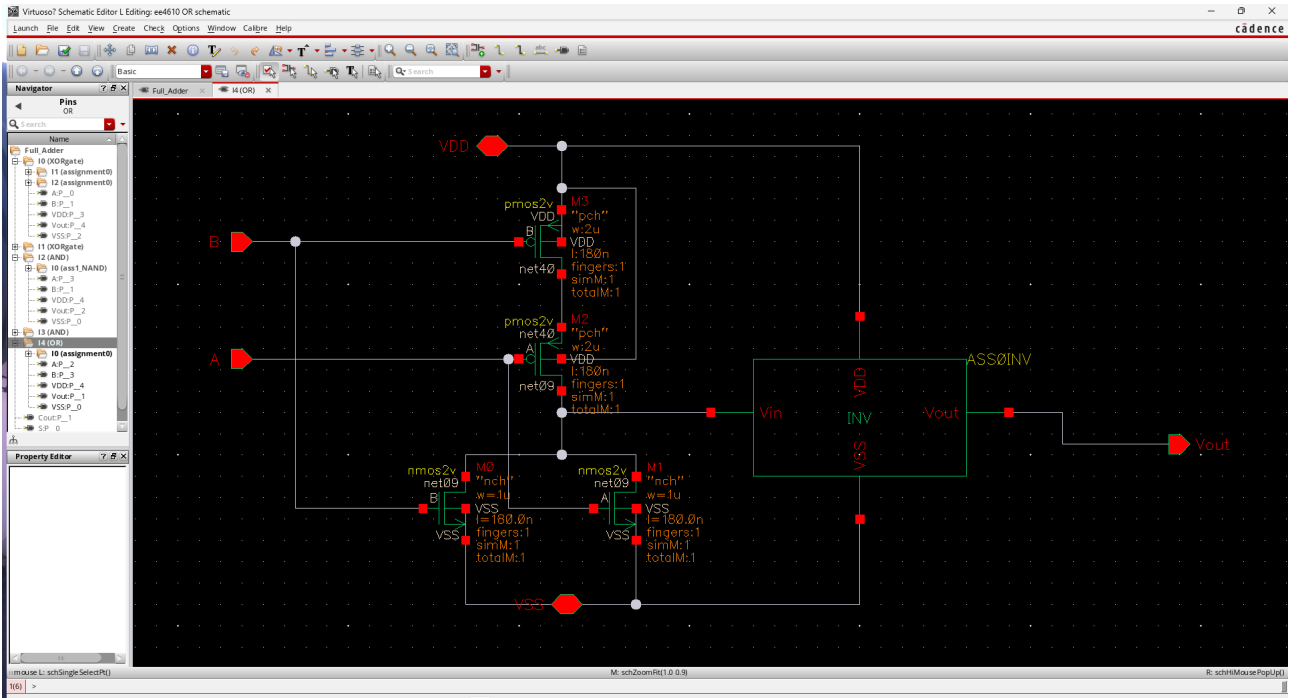


Figure 5: OR gate schematic.

2 Results

2.1 Propagation delay

We used the ADE L *Calculator* to automatically measure propagation delay and transition times from the transient waveforms. For example, to analyze the A-S route delay we applied these formulas:

```
delay?wf1 VT("/A") ?value1 0.9 ?edge1 "rising" ?nth1 1 ?td1 0.0 ?tol1 nil ?wf2 VT("/S") ?value2 0.9 ?edge2 "rising" ?nth2 1 ?tol2 nil ?td2 nil ?stop nil ?multiple nil
```

Figure 6: A-S t_{pLH} measurement expression.

```
delay?wf1 VT("/A") ?value1 0.9 ?edge1 "falling" ?nth1 1 ?td1 0.0 ?tol1 nil ?wf2 VT("/S") ?value2 0.9 ?edge2 "falling" ?nth2 1 ?tol2 nil ?td2 nil ?stop nil ?multiple nil
```

Figure 7: A-S t_{pHL} formula.

```
delay?wf1 VT("/S"), ?value1 0.18, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 VT("/S"), ?value2 1.62, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop nil, ?multiple nil
```

Figure 8: A-S rising formula.

```
delay?wf1 VT("/S"), ?value1 1.62, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 VT("/S"), ?value2 0.18, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop nil, ?multiple nil
```

Figure 9: A-S falling formula.

The same measurement expressions were reused for each path, changing only the input and output node names. And each delay analysis are using the signal with 2ms as period duty cycle.

2.1.1 A-S route

Outputs					
	Name/Signal/Expr	Value	Plot	Save	Save Options
1	A		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2	B		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3	C		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4	S		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
5	Cout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
6	A-S_tplh	249.2p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
7	A-S_tphl	222.898p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
8	A-S_rising	83.2516p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
9	A-S_falling	78.1663p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Figure 10: A-S propagation delay

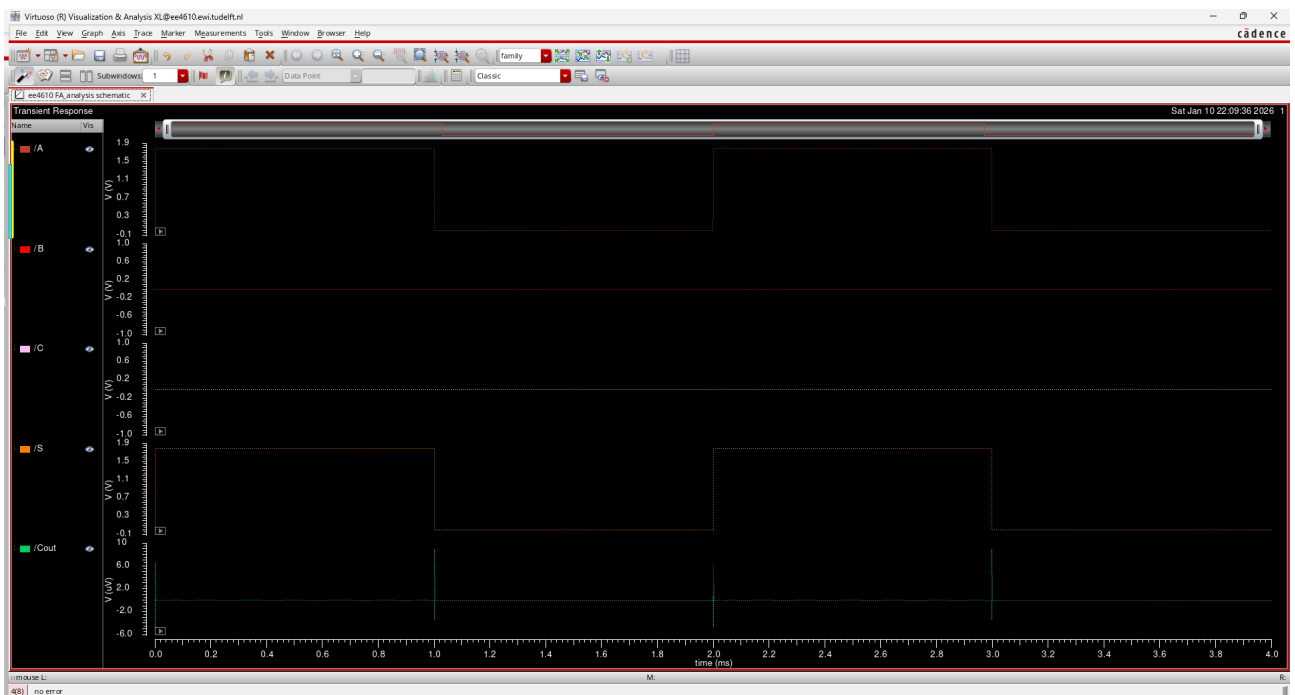


Figure 11: A-S propagation delay curve

The propagation delay of A-S route is:

$$t_{p(A-S)} = \frac{t_{pLH} + t_{pHL}}{2} = 236.049ps$$

2.1.2 B-S route

Outputs					
	Name/Signal/Expr	Value	Plot	Save	Save Options
1	A		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2	B		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3	C		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4	S		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
5	Cout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
6	B-S_tph	252.986p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
7	B-S_tphl	230.043p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
8	B-S_rising	83.2271p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
9	B-S_falling	78.0292p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Figure 12: B-S propagation delay

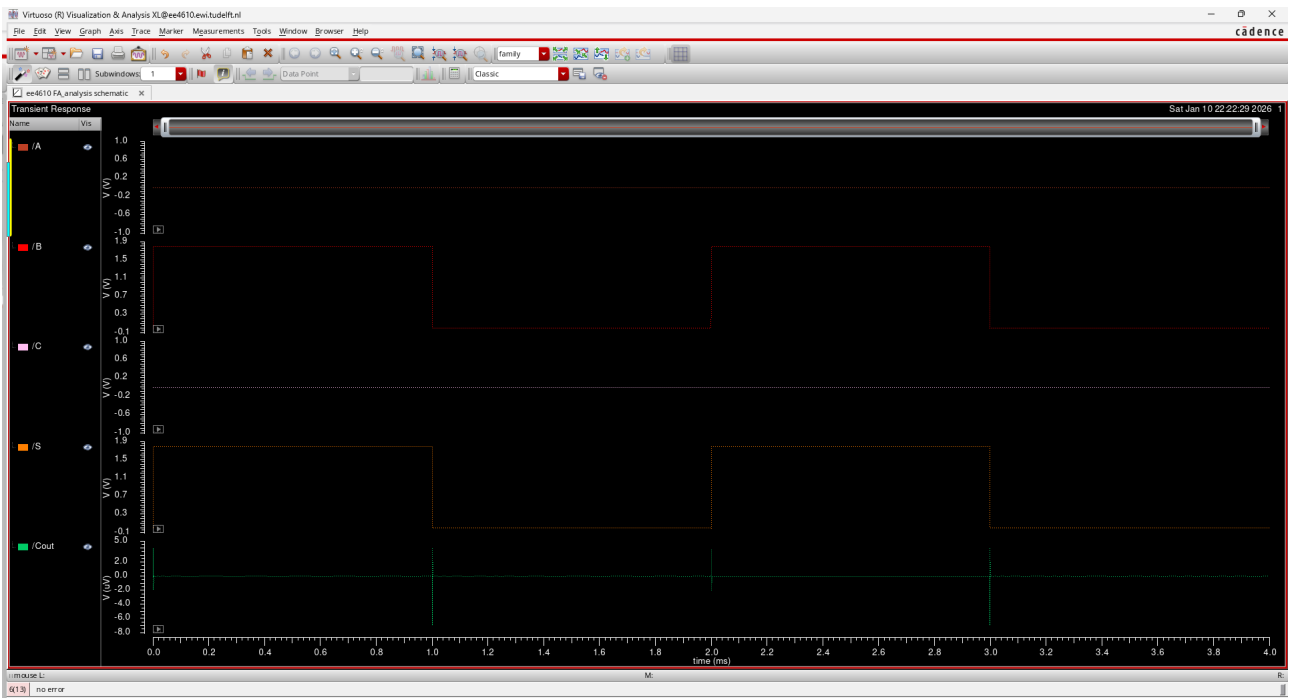


Figure 13: B-S propagation delay curve

The propagation delay of B-S route is:

$$t_{p(B-S)} = \frac{t_{pLH} + t_{pHL}}{2} = 241.708ps$$

2.1.3 C-S route

Outputs					
	Name/Signal/Expr	Value	Plot	Save	Save Options
1	A		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2	B		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3	C		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4	S		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
5	Cout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
6	C-S_tph	103.549p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
7	C-S_tphl	99.6081p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
8	C-S_rising	87.0622p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
9	C-S_falling	79.2009p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Figure 14: C-S propagation delay

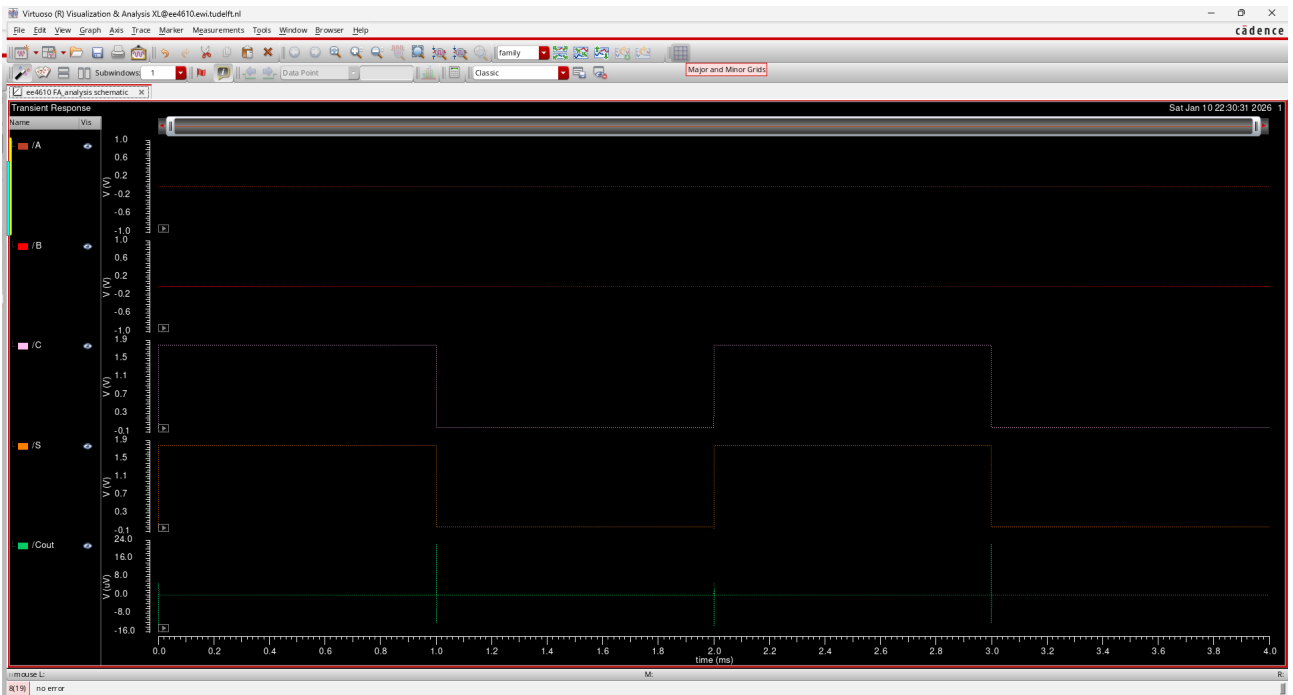


Figure 15: C-S propagation delay curve

The propagation delay of C-S route is:

$$t_{p(C-S)} = \frac{t_{pLH} + t_{pHL}}{2} = 101.579ps$$

2.1.4 A-Cout short route

Signal 'A' and signal 'B' will go through gate 'AND' and gate 'OR' to output.

Outputs					
	Name/Signal/Expr	Value	Plot	Save	Save Options
1	A		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2	B		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3	C		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4	S		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
5	Cout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
6	A-Cout_short_tplh	135.763p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
7	A-Cout_short_tphl	151.982p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
8	A-Cout_short_rising	23.7699p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
9	A-Cout_short_falling	25.1096p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Figure 16: A-Cout short route propagation delay

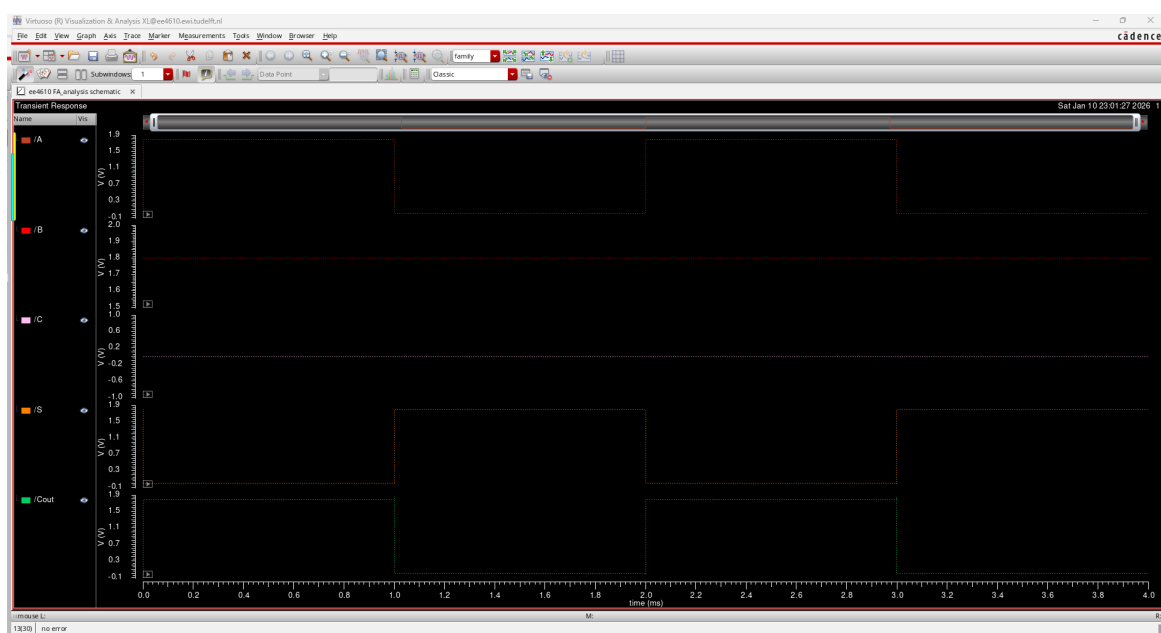


Figure 17: A-Cout short route propagation delay curve

The propagation delay of A-Cout short route is:

$$t_{p(A-Couts)} = \frac{t_{pLH} + t_{pHL}}{2} = 143.873ps$$

2.1.5 A-Cout long route

Signals 'A' and 'B' propagate through the XOR gate, then through the AND gate together with signal 'C', and finally through the OR gate to produce *Cout*.

Outputs					
	Name/Signal/Expr	Value	Plot	Save	Save Options
1	A		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2	C		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3	B		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4	S		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
5	Cout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
6	A-Cout_long_tplh	296.628p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
7	A-Cout_long_tphl	272.646p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
8	A-Cout_long_rising	21.9158p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
9	A-Cout_long_falling	25.0259p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Figure 18: A-Cout long route propagation delay

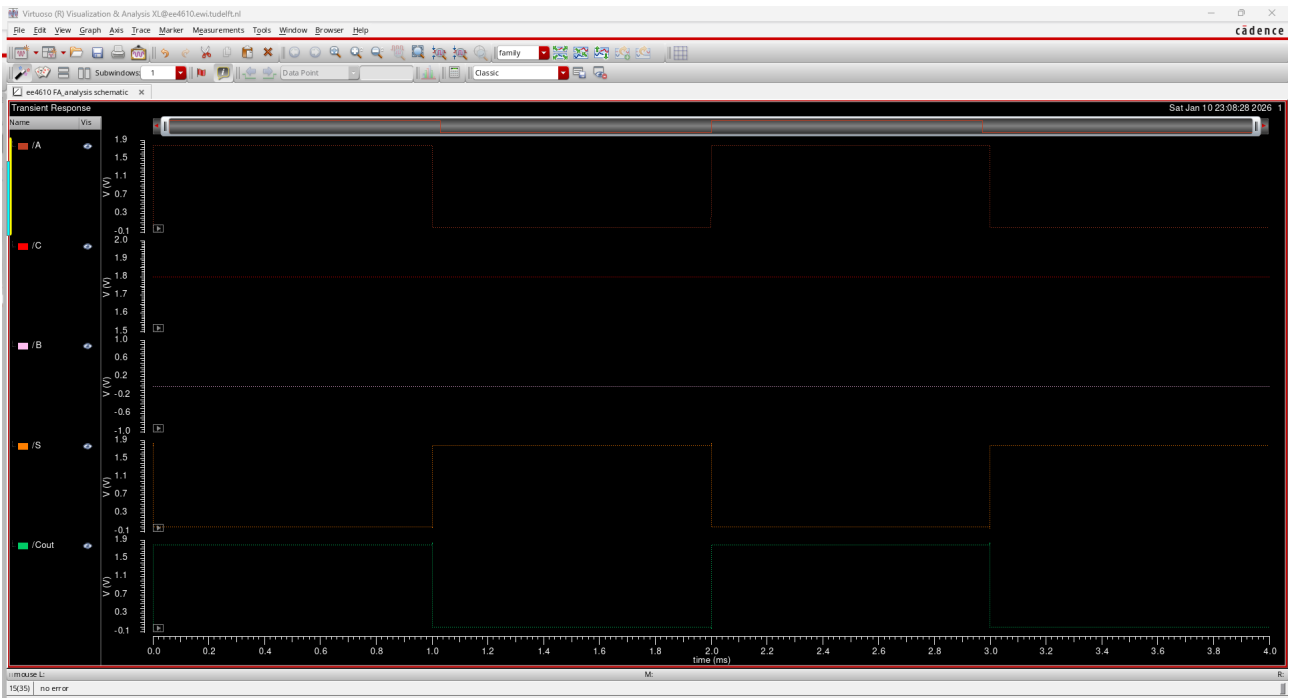


Figure 19: A-Cout long route propagation delay curve

The propagation delay of A-Cout long route is:

$$t_{p(A-Coutl)} = \frac{t_{pLH} + t_{pHL}}{2} = 284.637ps$$

2.1.6 C-Cout route

Outputs					
	Name/Signal/Expr	Value	Plot	Save	Save Options
1	A		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2	B		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3	C		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4	S		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
5	Cout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
6	C-Cout_tplh	130.816p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
7	C-Cout_tphl	141.866p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
8	C-Cout_rising	21.8998p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
9	C-Cout_falling	24.9064p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Figure 20: C-Cout propagation delay

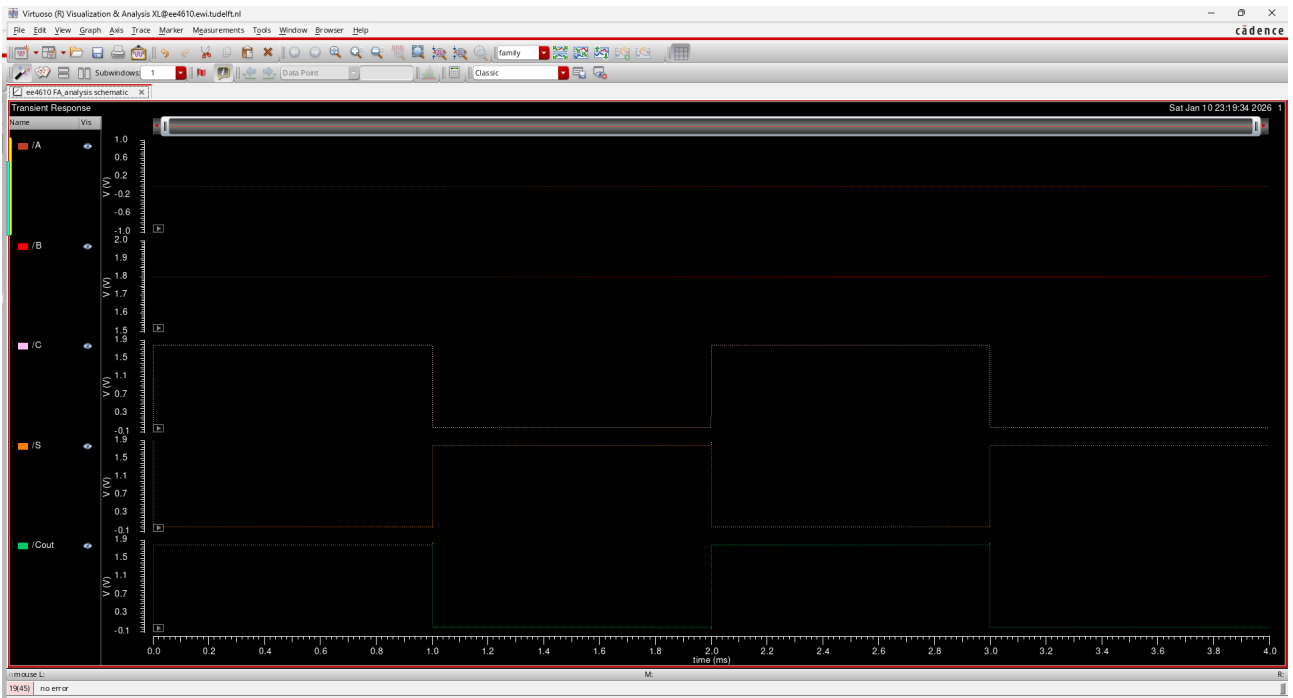


Figure 21: C-Cout propagation delay curve

The propagation delay of C-Cout route is:

$$t_{p(C-Cout)} = \frac{t_{pLH} + t_{pHL}}{2} = 136.341ps$$

2.1.7 Data analysis

To conclude the delay analysis result is:

Table 1: Propagation delay

Item	Value
$t_{pd}(A-S)$	236.049 ps
$t_{pd}(B-S)$	241.708 ps
$t_{pd}(C-S)$	101.579 ps
$t_{pd}(A-Couts)$	143.873 ps
$t_{pd}(A-Coutl)$	284.637 ps
$t_{pd}(C-Cout)$	136.341 ps
$t_{pd(max)}$	284.637 ps

Table 2: Rising time

Item	Value
$t_r(A-S)$	83.252 ps
$t_r(B-S)$	83.227 ps
$t_r(C-S)$	87.062 ps
$t_r(A-Couts)$	23.770 ps
$t_r(A-Coutl)$	21.916 ps
$t_r(C-Cout)$	21.899 ps
$t_{r,S(max)}$	87.062 ps
$t_{r,Cout(max)}$	23.770 ps

Table 3: Falling time

Item	Value
$t_f(A-S)$	78.166 ps
$t_f(B-S)$	78.029 ps
$t_f(C-S)$	79.201 ps
$t_f(A-Couts)$	25.196 ps
$t_f(A-Coutl)$	25.026 ps
$t_f(C-Cout)$	24.906 ps
$t_{f,S(max)}$	79.201 ps
$t_{f,Cout(max)}$	25.196 ps

2.2 Quiescent power

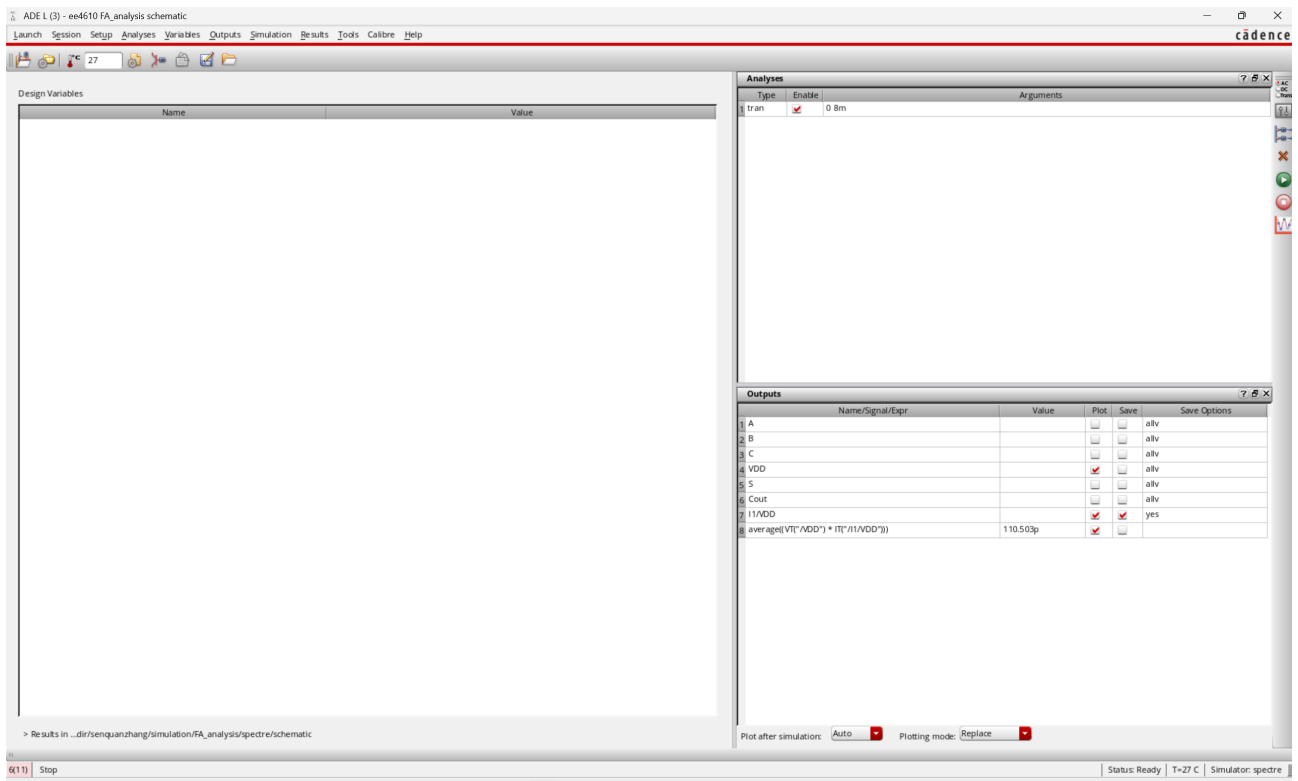


Figure 22: Quiescent power result

$$P_q = average(p(t)) = average(V \times I) = 110.503pW$$

2.3 Dynamic power

$$P_{\text{dyn}} = V_{\text{DD}}(I_{\text{avg,switch}} - I_{\text{avg,static}})$$

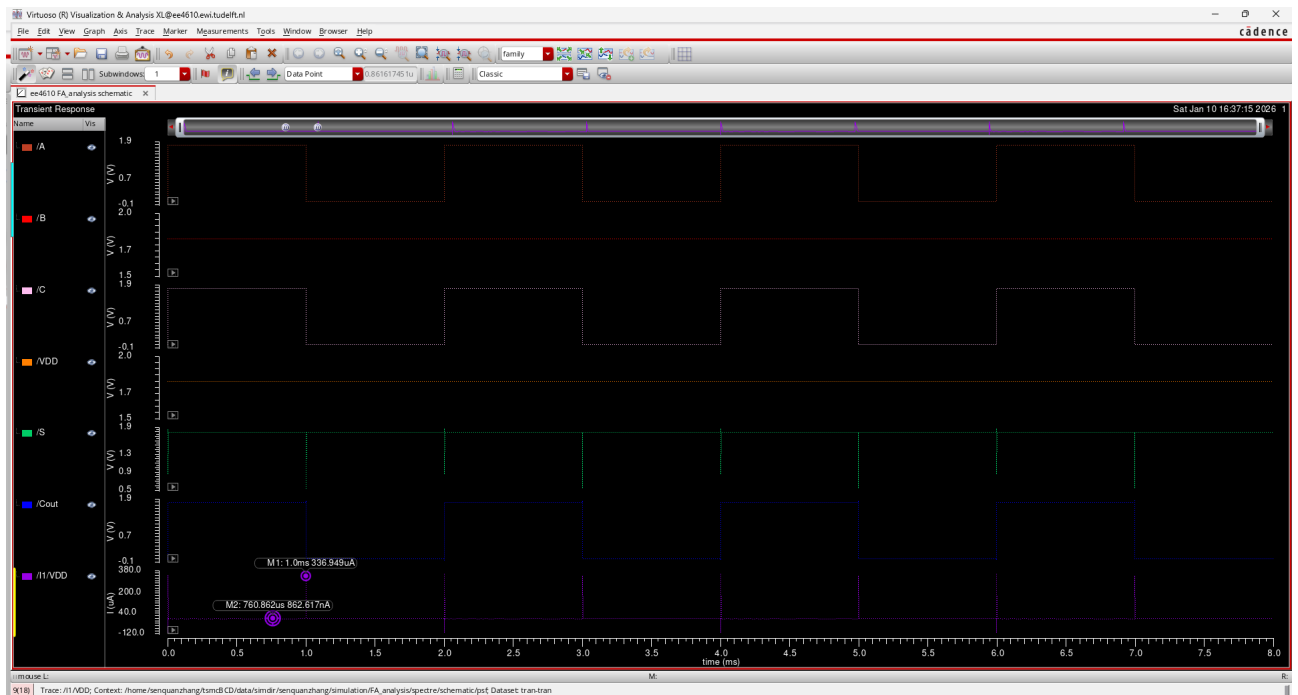


Figure 23: Dynamic power output curve

$$I_{\text{avg,switch}} = 336.949\mu A$$

$$I_{\text{avg,static}} = 862.617nA$$

$$P_{\text{dyn}} = V_{\text{DD}}(I_{\text{avg,switch}} - I_{\text{avg,static}}) = 604.955\mu W$$