

Assignment 1

DIGITAL IC DESIGN I

EE4610

Authors:

Daniel Tyukov (5714699)
Senquan Zhang (6338216)
Yaonan Hu (6573657)

January 13, 2026

Contents

Introduction	2
1 Schematic	2
1.1 Details of the NAND:	2
1.2 Schematic design about our NAND and symbol:	2
1.3 Test-bench design:	2
1.4 Input signals and power supply:	3
1.5 NAND circuit function validation:	3
1.6 Propagation delay and rising time & falling time analysis:	4
1.7 Power analysis:	6
1.7.1 Quiescent power:	6
1.7.2 Dynamic power:	7
2 Layout	8
2.1 Details of the POMS and NMOs	8
2.2 Schematic	8
3 Layout	8
3.1 DRC errors	9

Introduction

The last three digits of the student numbers are 6, 7, and 9. Hence, the widths of the PMOS and the NMOS should be as follows:


$$W_p = (9 + 6 + 7) \bmod 3 + 1 = 2 [\mu m], W_n = 0.5W_p = 1 [\mu m] \quad (1)$$

1 Schematic


1.1 Details of the NAND:

PMOS: width=2 μm ; length=180 nm ; NMOS: width=1 μm ; length=180 nm

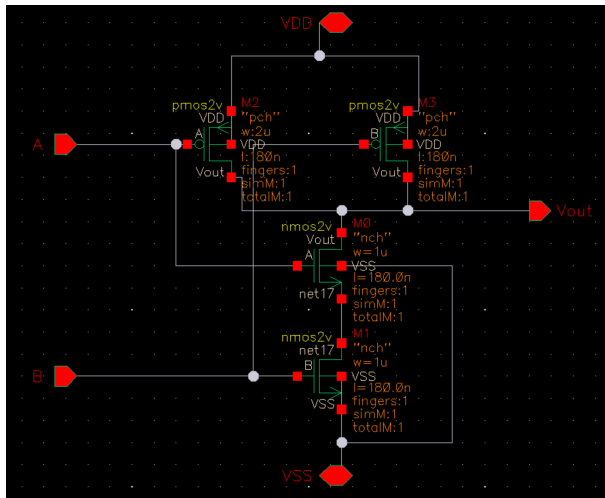1.2 Schematic design about our NAND and symbol:



(a) Schematic of NAND

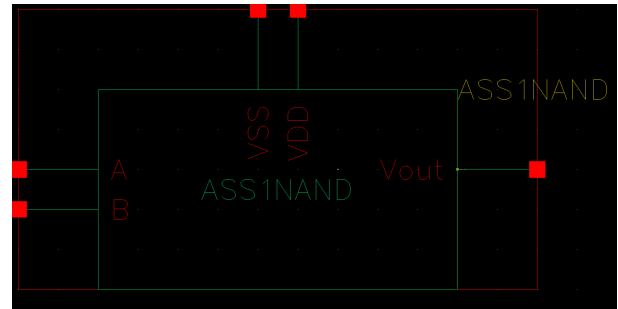

(b) Symbol of NAND

Figure 1: Propagation delay calculation settings

1.3 Test-bench design:

We add a capacitor after the 'Vout' to suppressing high-frequency spikes.

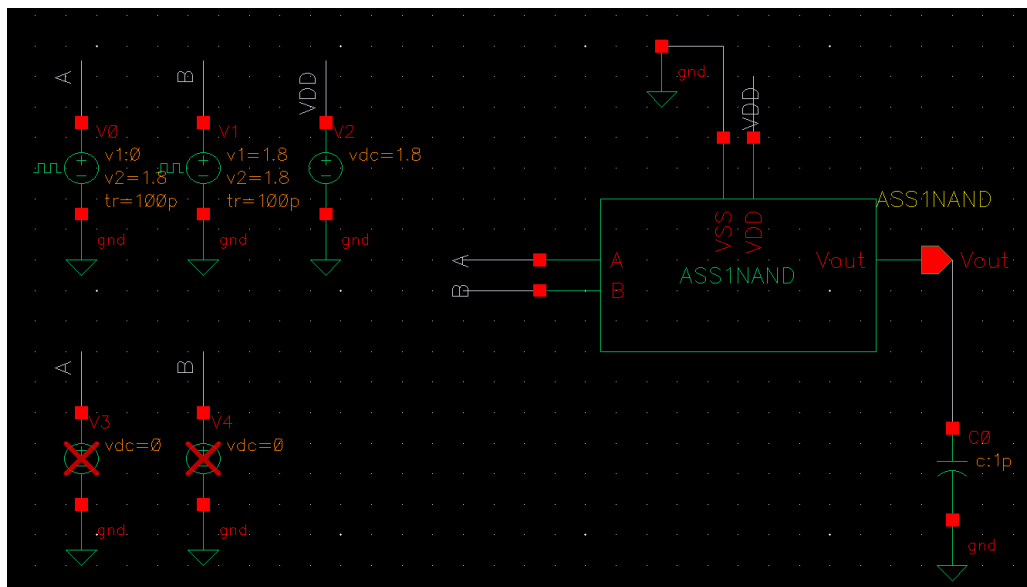


Figure 2: Test-bench design

1.4 Input signals and power supply:

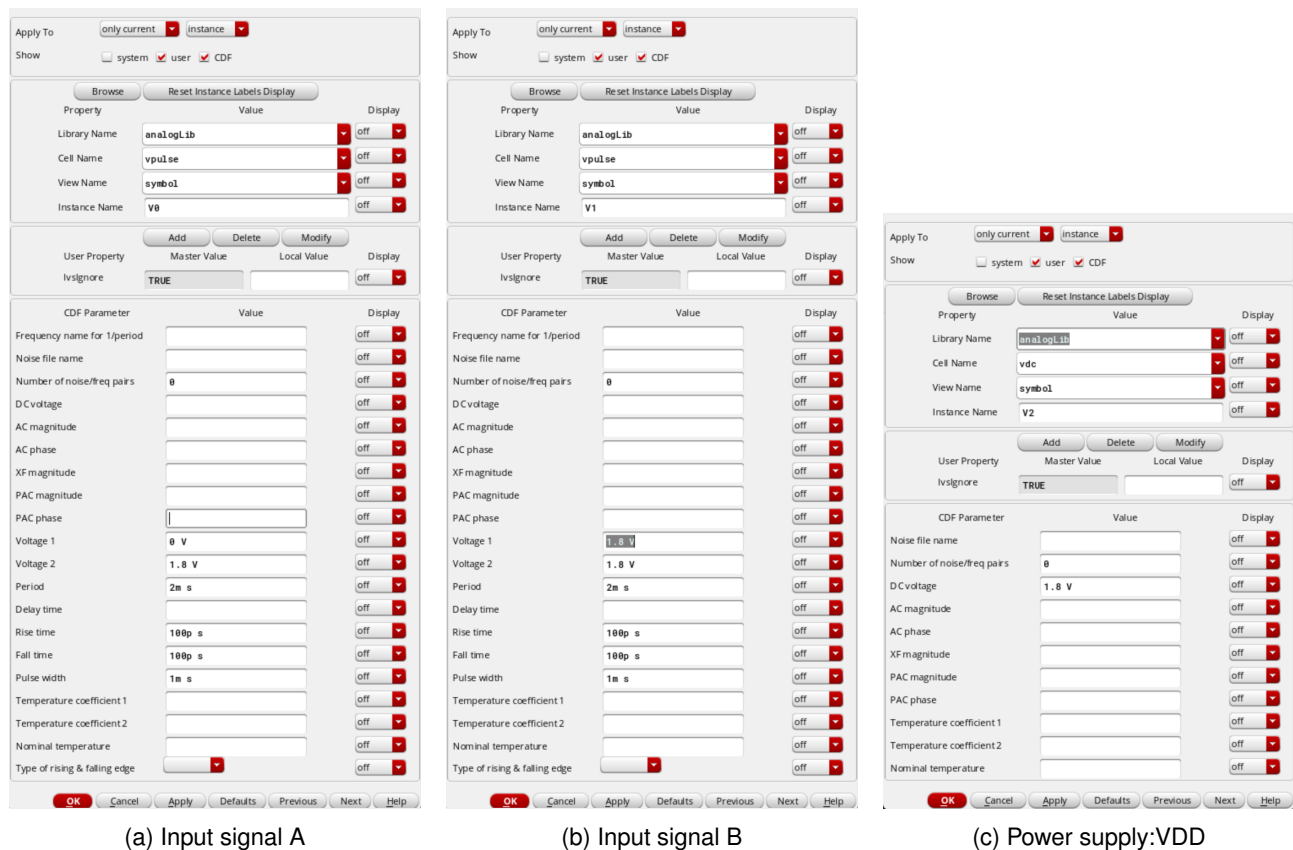


Figure 3: Input signals and power supply settings

1.5 NAND circuit function validation:

To validate the function of our NAND logic circuit. We use '1010' as input signal A and '1100' as input signal B. The expected output is '0111'.

 


Figure 4: Test-bench design

From the simulation result, we can say that the function of our NAND logic circuit is validated.

1.6 Propagation delay and rising time & falling time analysis:

 



Figure 5: Delay analysis output

From definition, we use $50\%V_{DD} = 0.9V$ as threshold voltage.


$$t_{pHL} = t(V_{out} = 0.5 V_{DD}) - t(V_{in} = 0.5 V_{DD})$$

$$t_{pLH} = t(V_{out} = 0.5 V_{DD}) - t(V_{in} = 0.5 V_{DD})$$

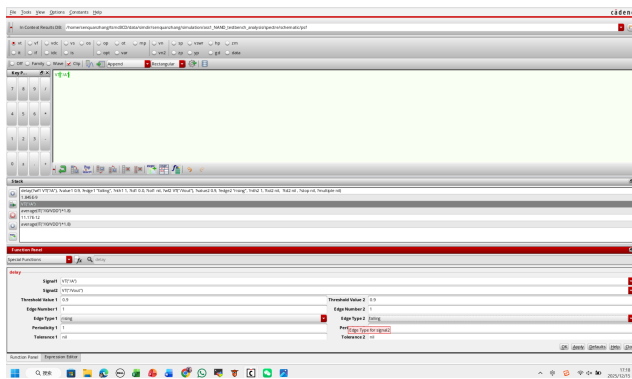To analysis ' t_{pHL} ' and ' t_{pLH} ', we used the 'calculator' tool in the 'ADE L' simulation. We set the 'function' with 'delay' as showed in following figures.



(a) t_{pHL} calculation setting

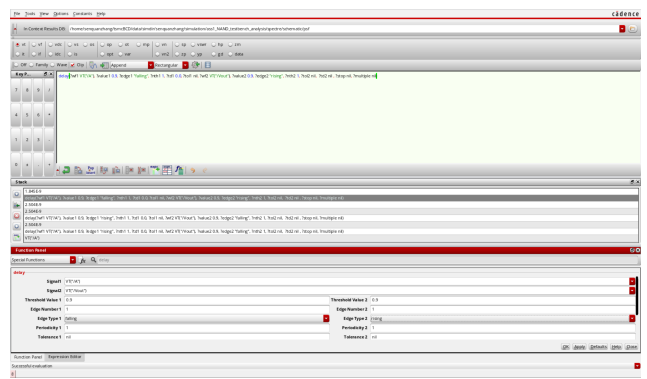


(b) t_{pLH} calculation setting

Figure 6: Propagation delay calculation settings


We also used the same way to analysis the rising time & falling time. But in rising time & falling time analysis, the threshold voltages are $10\%V_{DD} = 0.18V$ and $90\%V_{DD} = 1.62V$.

$$t_r = t(V_{out} = 0.9 V_{DD}) - t(V_{out} = 0.1 V_{DD})$$
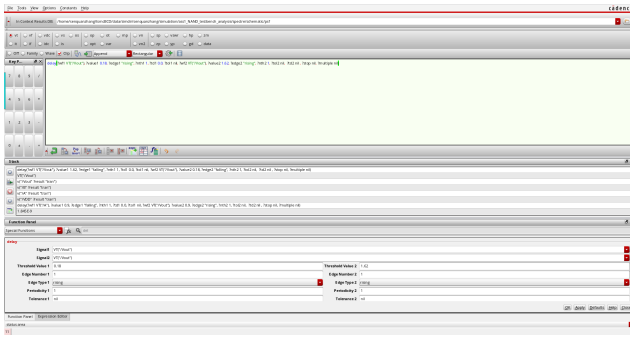
$$t_f = t(V_{out} = 0.1 V_{DD}) - t(V_{out} = 0.9 V_{DD})$$



(a) Rising time calculation setting

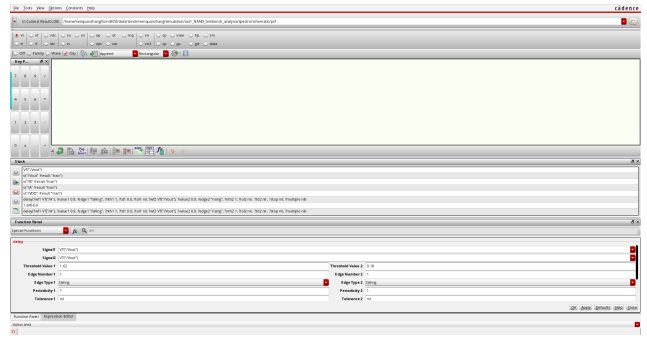

(b) Falling time calculation setting

Figure 7: Propagation delay calculation settings

The result of the simulation is:

Analyses				
Type	Enable	Arguments		
1 tran	<input checked="" type="checkbox"/>	0 3m moderate		

Outputs				
Name/Signal/Expr	Value	Plot	Save	Save Options
1 A		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2 B		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3 Vout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4 tph	1.84479n	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
5 tphi	2.50449n	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
6 rising_time	3.80295n	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
7 falling_time	4.83167n	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Figure 8: Propagation time and rising time & falling time simulation result)

Then the propagation delay is:

$$t_p = \frac{t_{pLH} + t_{pHL}}{2} = 2.17464ns$$

To conclude the delay analysis result is:

Item	Value
t_p	2.17464 ns
t_r	3.80295 ns
t_f	4.83167 ns

Table 1: Delay analysis results.

1.7 Power analysis:

1.7.1 Quiescent power:

$$P_q = \text{average}(p(t)) = \text{average}(V \times I)$$

Quiescent power of our circuit is 11.169 pW:

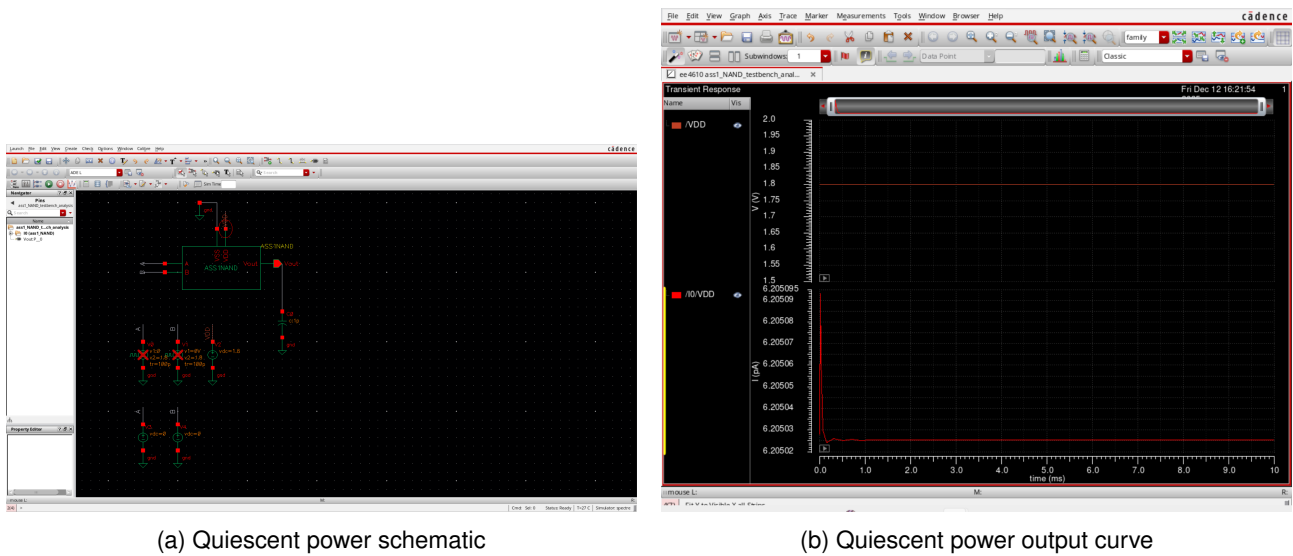


Figure 9: Input signals and power supply settings

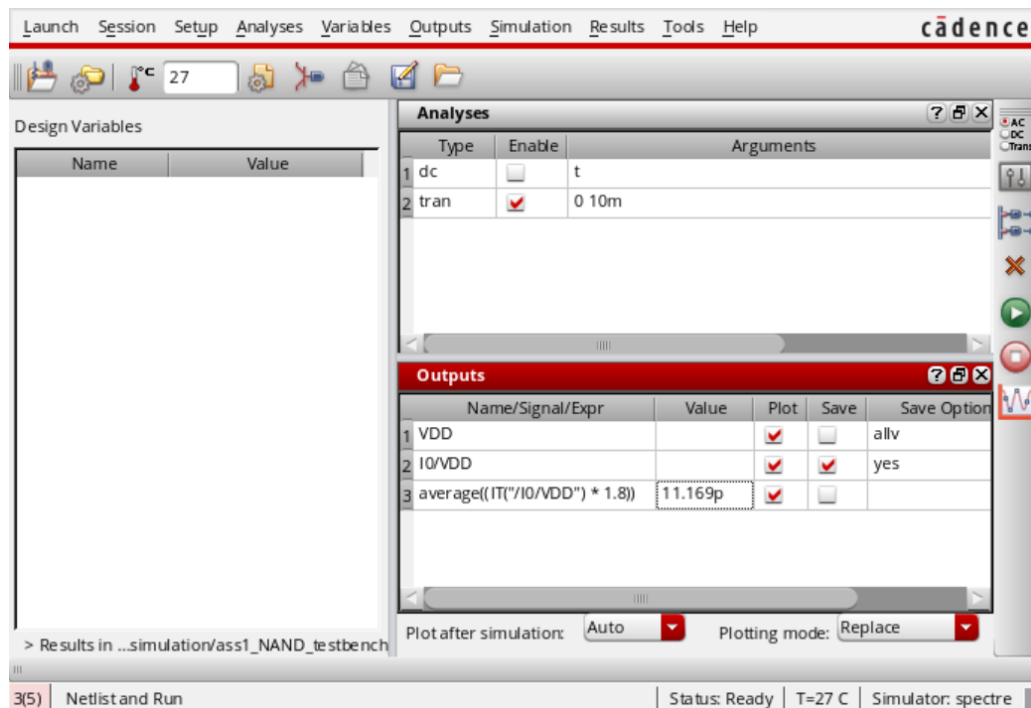


Figure 10: Quiescent power simulation result

1.7.2 Dynamic power:

$$P_{\text{dyn}} = V_{\text{DD}}(I_{\text{avg,switch}} - I_{\text{avg,static}})$$

In dynamic power analysis the test-bench is changed back to Figure 2

 


Figure 11: Dynamic power output curve

$$I_{\text{avg,switch}} = 553.157\mu A$$

$$I_{\text{avg,static}} = 24.4213pA$$

$$P_{\text{dyn}} = V_{\text{DD}}(I_{\text{avg,switch}} - I_{\text{avg,static}}) = 0.996 \times 10^{-4} W$$

2 Layout

2.1 Details of the POMS and NMOs

PMOS: width: 2 μm , length 0.18 μm .

NMOS: width: 1 μm , length 0.18 μm .

The value of width was calculated by the given formula in the assignment guide. Moreover, the length is the minimum length (0.18 μm) given by the assignment slides.

2.2 Schematic

The schematic is labeled differently but the architecture of the NAND gate and bias voltage are the the same as the first section. The schematic can be found in Fig.12.

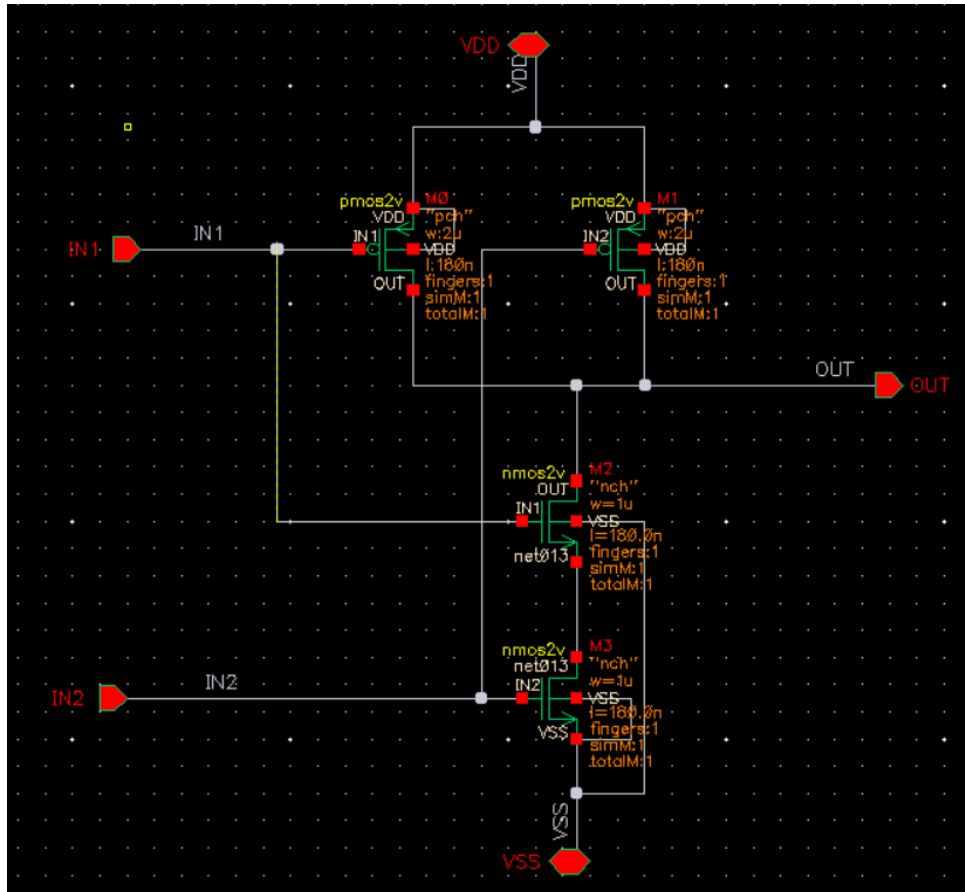


Figure 12: Schematic of NAND used by the layout

3 Layout

The layout with highlighted size can be found in Fig.13.

 


Figure 13: Layout with labeled width

3.1 DRC errors

The DRC errors can be found in Fig.14.

Check / Cell	R
Check NBL.R.1	2
Check PO.R.4	4
Check PO.R.3	1
Check M1.R.1	1
Check M2.R.1	1
Check M3.R.1	1
Check M4.R.1	1
Check M5.R.1	1
Check UTM30K.R.1	1
Check DRMR.1	1
Check PO.R.5	1
Check OD.R.3	1
Check MOM.R.2	1

NBL.R.1 { @ LV device must be isolated by NBL combine with HVM4.
 B = (FP AND NHEL) AND BUTLUMMY
 A = (((((LV_DEVICES NOT INTERACT RNHEL) NOT INTERACT B) NOT INTERACT SV_LowR_PGATE) NOT INTERACT
 SV_LowR_SLIT_PGATE) NOT INTERACT SV_SLIT_PGATE) NOT INTERACT SVNH_DIO
 A NOT INSIDE NBL1

Figure 14: DRC errors of the layout